

LAB 5: HIERARCHIAL DESIGN AND FORMAL VERIFICATION

Adam Sumner

Illinois Institute of Technology

ECE 429-01

Lab Date: October 14th, 2015

Due Date: October 21st, 2015

1 Introduction

The purpose of this lab is to introduce the student to hierarchical design and formal verification techniques that are essential when constructing complex circuits. A layout for a 2-input NAND gate will be built, and then a 2 input AND gate will be constructed using the schematics built from previous labs.

2 Theory/Pre-Lab

2.1 Theory

Since chip fabrication can be incredibly costly, it is a must to verify that the design will work correctly before sending it out for tapeout. Verifying functionality is one of the many important tasks that validates the success of a specific chip's design. While it is possible to give specific input to validate the functionality, there could potentially be a high number of inputs, producing hundreds of possibilities for output. Manual verification can become tedious and a waste of time. To resolve this issue, formal verification techniques have been proposed which can provide evidence for the functional correctness of a design. One such methodology is called equivalence checking. This technique takes two designs and verifies that both designs operate with the same functionality. LVS is one example of equivalence checking, as it shows where the layout is exactly the same as the schematic, while other factors such as transistor size are also verified. Because circuit designs can become complex, it's necessary to specify designs at a higher abstraction level. Due to the fact that the design in this lab is digital, boolean logic can be used for verification.

2.2 Pre-Lab

A stick diagram for a 2-input static CMOS NAND gate and a 2-input AND gate design were both sketched. They are shown in Figures 1 and 2.

 


Figure 1: Stick Diagram for Static CMOS 2-input NAND Gate

 


Figure 2: 2-input AND Gate Design

3 Implementation

3.1 Schematics

 


Figure 3: 2-input NAND Gate Layout

 


Figure 4: 2-input And Gate Schematic

 


Figure 5: 2-input AND Gate Layout

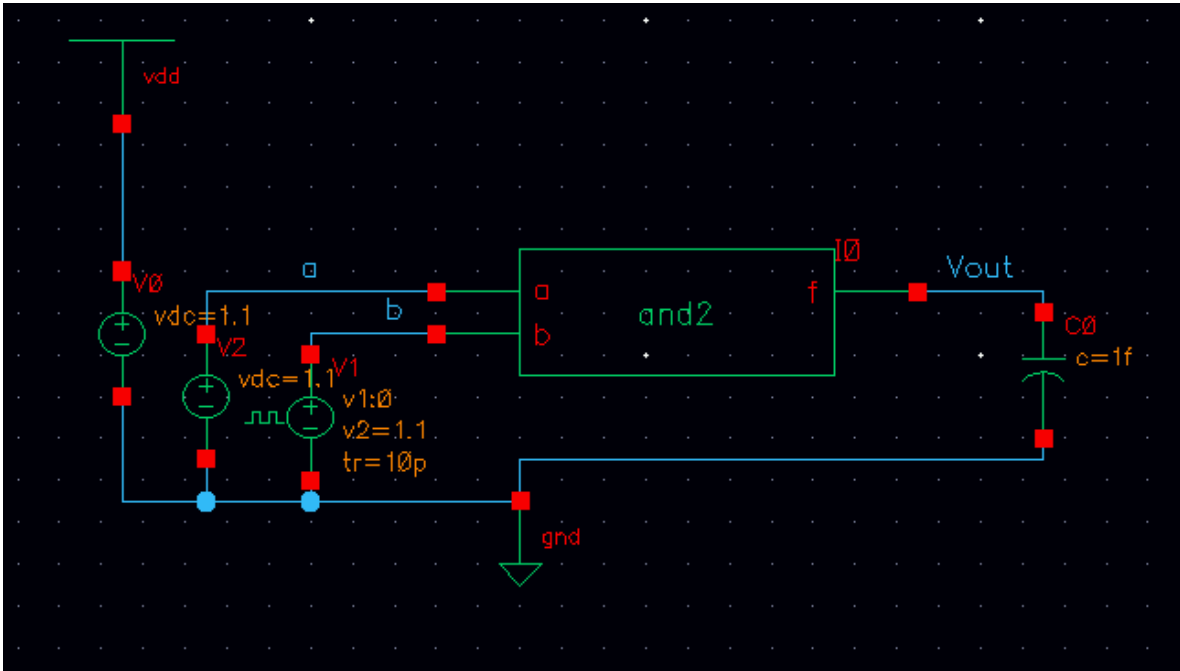


Figure 6: Test Circuit for 2-input AND Gate

```

1 module and2(a,b,f);
2   input a,b;
3   output f;
4   assign f=a&b;
5 endmodule

```

Figure 7: Verilog Model Code

3.2 Procedure

A NAND gate layout was created in Virtuoso and was verified using LVS. After this, a 2-input AND gate was designed using both the schematic and layout view. This was then verified using LVS, and it was also verified against the verilog model. Delay was then calculated for the AND gate design.

3.3 Results

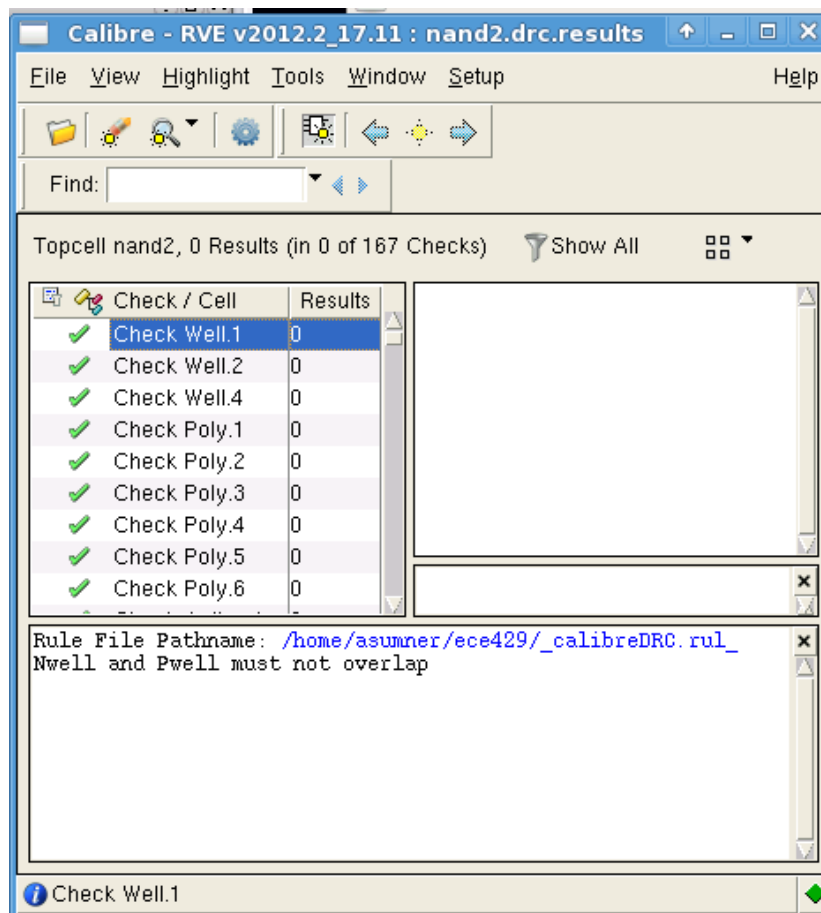


Figure 8: 2-input NAND Gate DRC Results

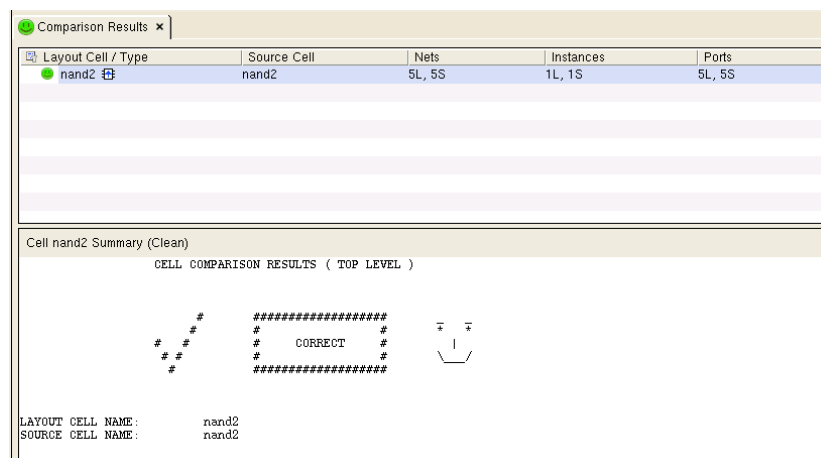


Figure 9: 2-input NAND Gate LVS Results

Topcell and2, 0 Results (in 0 of 167 Checks) Show All ☐		
Check / Cell	Results	
✓ Check Well.1	0	
✓ Check Well.2	0	
✓ Check Well.4	0	
✓ Check Poly.1	0	
✓ Check Poly.2	0	
✓ Check Poly.3	0	
✓ Check Poly.4	0	
✓ Check Poly.5	0	
✓ Check Poly.6	0	

Rule File Pathname: [/home/asummer/ece429/_calibreDRC.rul_](#)
 Nwell and Pwell must not overlap

Figure 10: 2-input AND Gate DRC Results

Comparison Results ×		
Layout Cell / Type	Source Cell	Nets
● and2 ⚙	and2	6L, 6S

Cell and2 Summary (Clean)		
CELL COMPARISON RESULTS (TOP LEVEL)		
# # # #	<pre> ##### # # # CORRECT # # # ##### </pre>	<pre> + + +---+ </pre>
LAYOUT CELL NAME:	and2	
SOURCE CELL NAME:	and2	

Figure 11: 2-input AND Gate LVS Results

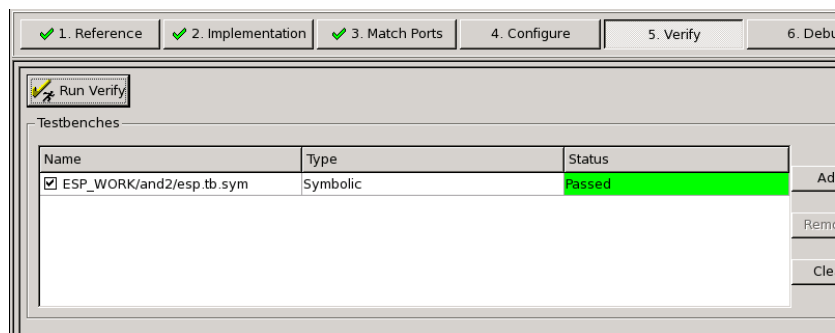


Figure 12: Verilog Equivalence Validated

 


Figure 13: 10 \rightarrow 11 Delay Measurements

 


Figure 14: 01 \rightarrow 11 Delay Measurements

 


Figure 15: 00 \rightarrow 11 Delay Measurements

w=90nm l=50nm	Transition		
	10→11	01→11	00→11
Rising Propagation Delay	17.656e-12 s	19.095e-12 s	18.665e-12 s
Falling Propagation Delay	19.615e-12 s	22.491e-12 s	14.797e-12 s
Average Power Consumption	3.17-05 W	3.26e-05 W	3.23e-05 W

Table 1: Delay and Power Consumption of Each Excitation with 1f Load Capacitance

3.4 Discussion

Upon analysis of the results, it is clear that both a 2-input NAND Gate layout was successfully constructed, along with a 2-input AND Gate layout and schematic. Figures 8-12 show the validity of the equivalence checks while Figures 13-15 show the measurements of the delay. The results obtained are accurate and show that using previously created schematics, AND gate functionality was successfully obtained.

3.5 Questions

1. **Is there any other way to design an AND gate than combining an inverter with a NAND gate? Which one will you prefer?** Yes, it is possible to design an AND gate by using a 2-input NAND gate and then connecting its output to both inputs of another 2-input NAND Gate. This essentially turns the functionality of the second NAND gate into an inverter, producing the AND functionality desired. The preferred method is to use a NAND gate and an inverter since it utilizes less transistors.
2. **Do the input transitions leading to the propagation delays match your expectations? Why or why not?** Yes, it was expected that the delays would be much longer than that of a regular NAND gate due to the complexity of this circuit.
3. **Is there any relationship between the propagation delays you measured in this lab for the AND gate and those you measured in Lab 2 for the inverter and in Lab 4 for the NAND gate?** Yes it seems that the delays were additive, which makes sense since the two logic gates are daisy chained together.
4. **What is the difference between a schematic and a Verilog model?** A Verilog model is a way to represent a circuit purely with code. This makes it incredibly easy to quickly construct and simulate circuits. A schematic physically shows the layout of the circuit, requiring some sort of gui design software to lay the gates out.

4 Conclusions

Overall the lab was a success. A 2-input NAND gate layout was successfully created, and it was used in conjunction with a previously created Inverter schematic to design AND Gate functionality. Furthermore, the design was successfully verified using both LVS and Verilog equivalence checking. The AND gate may now be used in future designs.