

LAB 8: CARRY-RIPPLE ADDITION III

Adam Sumner

Illinois Institute of Technology

ECE 429-01

Lab Date: November 2nd, 2015

Due Date: November 11th, 2015

1 Introduction

The purpose of this lab is to finalize the design of an adder circuit by combining both the previously designed layout and schematic of a one bit adder from previous labs. Specifically, this lab will tackle building a 4-bit adder circuit. This circuit will then be checked for its accurate functionality using LVS and verilog.

2 Theory/Pre-Lab

2.1 Theory

An adder circuit is one that is able to take two binary inputs and accurately calculate the sum. To implement this via circuitry, addition is done bit by bit. As discussed in the previous two experiments a mirror adder circuit design is an efficient way to perform one bit addition with carry. By combining 4 one bit adders, it's possible to add 4 bit numbers together. This is shown in Figure 1.

 


Figure 1: Four Bit Adder Diagram

2.2 Pre-Lab

The pre-lab involved reviewing the carry-ripple architecture discussed in Lab 6. The following two sets of inputs were also translated:

- 11+5
- 4+10

Their translation is shown in Figure 2.

$$\begin{array}{r|l}
 11 & 1011 \\
 + 5 & 0101 \\
 \hline
 16 & 10000
 \end{array}
 \qquad
 \begin{array}{r|l}
 4 & 0100 \\
 + 10 & 1010 \\
 \hline
 14 & 01110
 \end{array}$$

Figure 2: Pre-Lab Translation

3 Implementation

3.1 Schematics

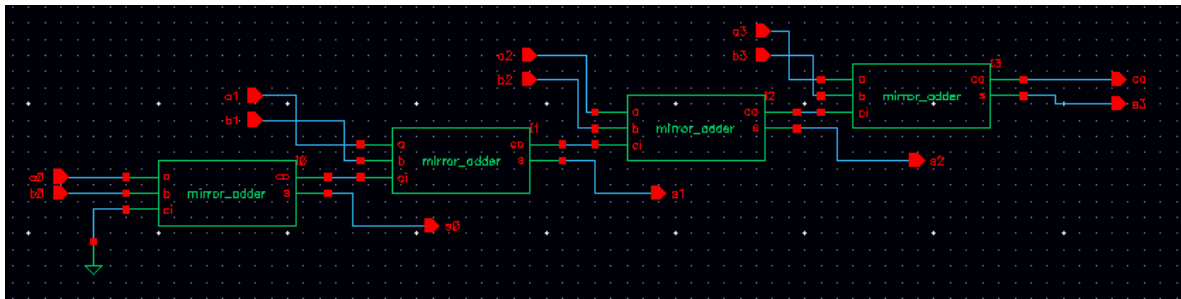


Figure 3: 4-bit Adder Schematic

 


Figure 4: 4-bit Adder Layout

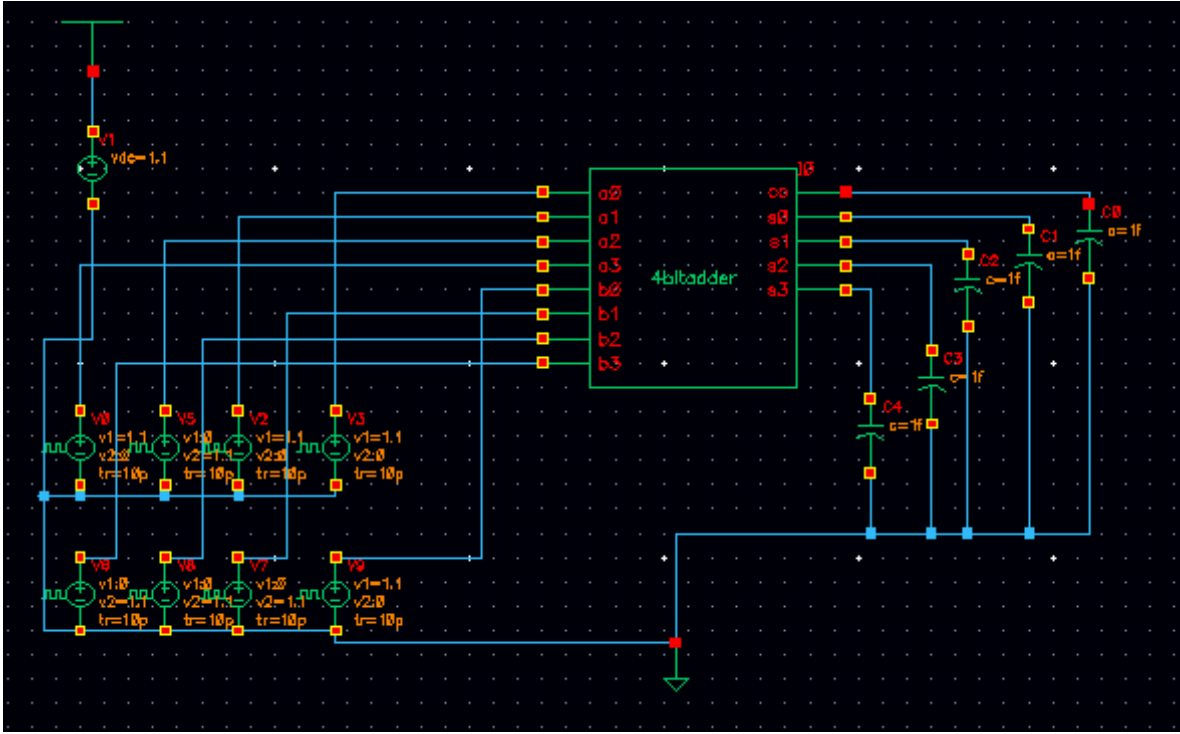


Figure 5: 4-bit Adder Test Circuit ($11 + 5 \rightarrow 4 + 10$)

```

1  module adder_4bit(A,B,S,CO);
2      input  [3:0] A,B;
3      output [3:0] S;
4      output CO;
5      assign {CO,S}={1'b0,A}+{1'b0,B};
6  endmodule

```

Figure 6: Verilog Code for 4-bit Adder Verification

```

1      module stimulus;
2          reg [3:0] A,B;
3          wire [3:0] S;
4          wire CO;
5
6          adder_4bit a(A,B,S,CO);
7
8          initial
9          begin
10             #10 A=4'b0000; B=4'b0000;
11             #5 $display ("%d+%d=%d %b", A,B,S,CO);
12
13             #10 A=4'b1011; B=4'b0101;
14             #5 $display ("%d+%d=%d %b", A,B,S,CO);
15
16             #10 A=4'b0100; B=4'b1010;
17             #5 $display ("%d+%d=%d %b", A,B,S,CO);
18
19             #10 A=4'b0001; B=4'b0001;
20             #5 $display ("%d+%d=%d %b", A,B,S,CO);
21
22             #10 A=4'b0001; B=4'b0111;
23             #5 $display ("%d+%d=%d %b", A,B,S,CO);
24
25             #10 A=4'b1000; B=4'b0111;
26             #5 $display ("%d+%d=%d %b", A,B,S,CO);
27         end
28     endmodule
29

```

Figure 7: Verilog Code for 4-bit Adder Verification

3.2 Procedure

The procedure of this lab involved first constructing the schematic and layout of the 4-bit adder. This is shown in Figures 3 and 4. LVS was then run to verify that they are both equivalent. After this, two verilog files shown in Figures 6 and 7 were created and verified using the command:

```
verilog adder4\ test.v adder4.v
```

Once this was done, ESP was run to check that the schematic functionality was the same of the verilog functionality. Once done, a test circuit was created to simulate 11+4 and 4+10. This is shown in Figure 5. Once all the functionality of the adder was

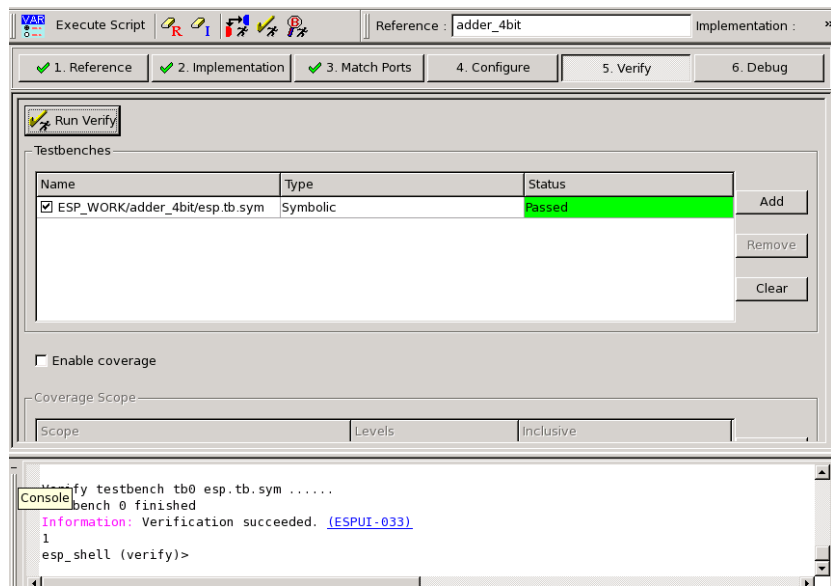


Figure 10: Equivalence Checking using ESP

 


Figure 11: S0 Delay

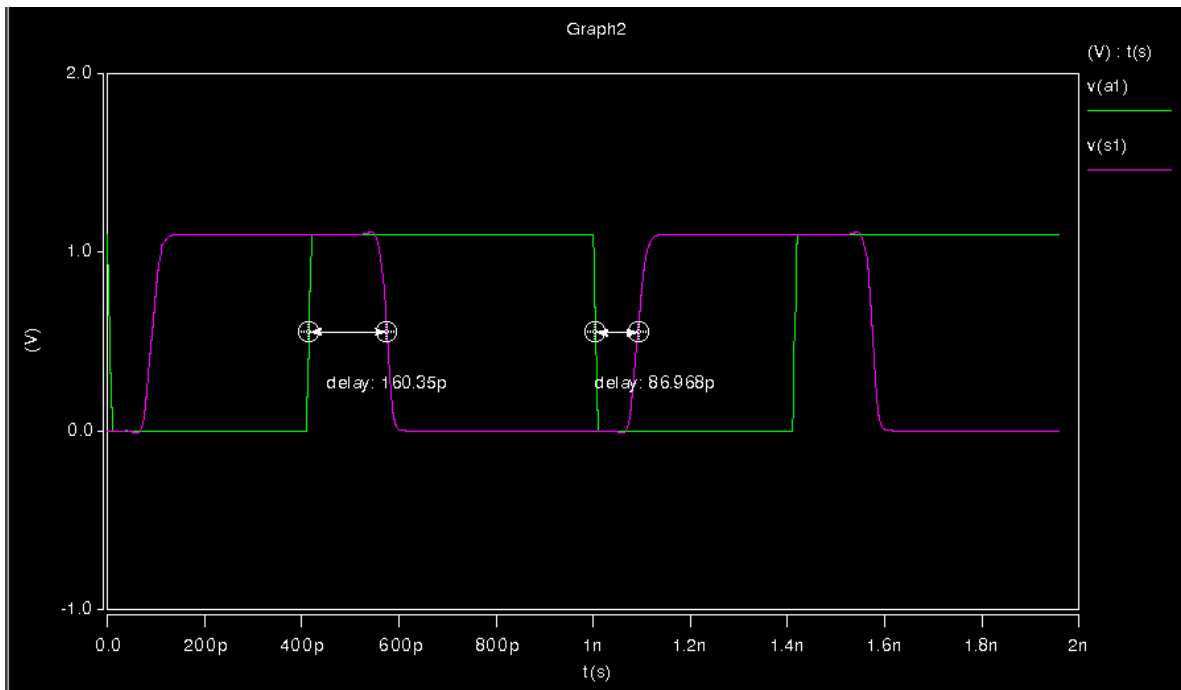


Figure 12: S1 Delay

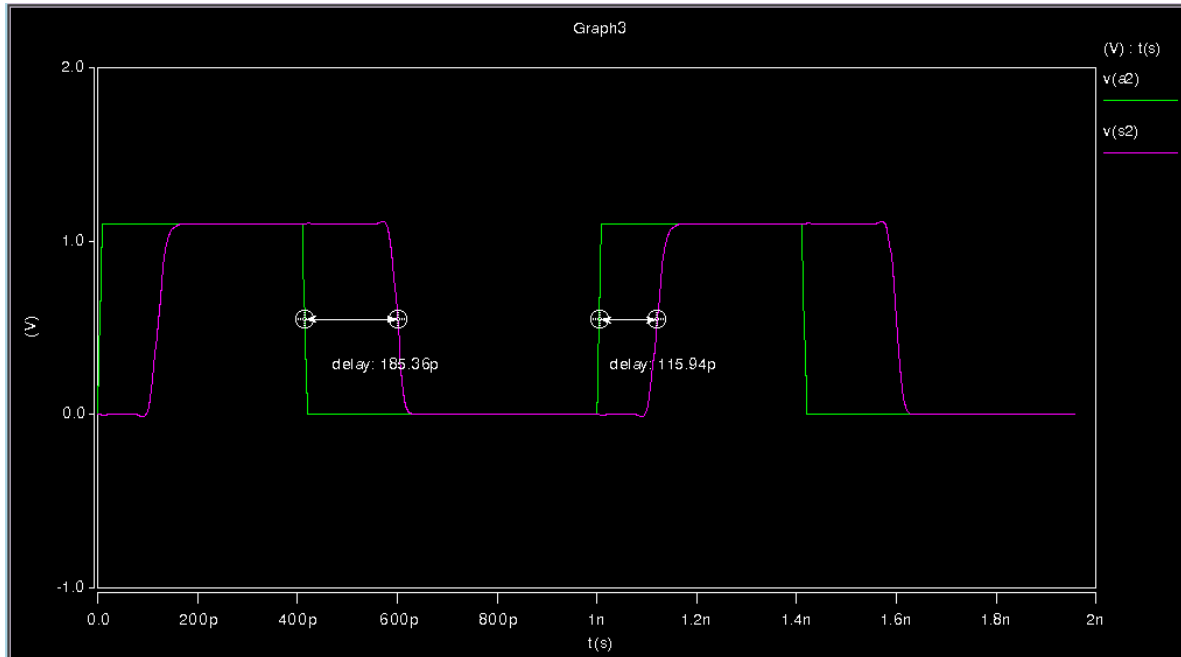


Figure 13: S2 Delay

 


Figure 14: S3 Delay

 


Figure 15: A0 and A1 CO Delay

 


Figure 16: A2 and A3 CO Delay

3.4 Discussion

As seen in Figures 8 to 10, all of the verification techniques performed were successful. The delay between A0-A3 and S0-S3 were also successfully measured and are shown in Figures 11 to 14. It should be noted that in the delay of S0, there is some noise generated when the DC pulse changes. The output of S0 should always be 0. Furthermore, the delay in CO was also measured successfully and is shown in Figures 15 and 16. On top of this data that was gathered, the results all verified that a 4 bit adder was successfully constructed.

How is the functionality of your adder design validated/verified at various abstraction levels?

The design is verified at three levels. First the code describing a 4 bit adder was written and verified by outputting the results of sample inputs. This is shown in Figure 8. The next level of the design that was verified is the Layout and Schematic level. This verified that both the layout designed and the schematic designed have the same functionality. This is shown in Figure 9. The last level that was checked was the verilog code vs the schematic. Since the verilog code was already verified to ensure the numbers were being added correctly, this checks that the schematic functions with the intended result. This is shown in Figure 10.

4 Conclusions

Overall this lab was a success. Over the course of three separate labs, a 4 bit adder was designed, tested, and can now be used in future designs.