

Homework 1

Adam Sumner
ECE 429

September 21st, 2015

1 Explain the Following Terminologies Briefly

- **Moore's Law** - The observation that the number of transistors in dense integrated circuits has doubled approximately every two years. Named after Gordon E. Moore
- **Feature Size** - The minimum dimension of a transistor that can be reliably built
- **VLSI Design for Power** - Discipline of design that aims to reduce power dissipations while maintaining adequate throughput rate
- **VLSI Design for Manufacturing** - Discipline of design that aims to produce a product in a timely manner with sufficient yield to be profitable
- **ASIC** - Application-Specific Integrated Circuit. An integrated circuit customized for a particular use, rather than general-purpose use
- **Logical Synthesis** - Process by which an abstract form of circuit behavior (usually represented at RTL) is turned into a design implementation
- **Physical Synthesis** - Step in the design cycle that converts circuit representations of components into geometric representations of shapes which, when they are manufactured in their corresponding layers, will ensure the correct functionality
- **Dynamic Power and Leakage Power** - The power consumed during the switching of a transistor, and the power lost to leakage current of transistors
- **Conduction Band** - The lowest range of vacant electronic states. Determines conductivity of the solid
- **Valence Band** - The highest range of electron energies in which electrons are normally present at absolute zero. Determines conductivity of the solid
- **Velocity Saturation** - State of a semiconductor when the carrier velocity reaches a maximum value
- **Subthreshold Conduction** - The current between the source and drain of a MOSFET when the transistor is in the subthreshold region

- **Hot Carriers** - Electrons in a solid-state electronic device that gains sufficient kinetic energy to overcome a potential barrier in order to break an interface state
- **MOSFET Operation Regions** - Three separate modes of a MOSFET depending on the voltage at the terminals: Cutoff, Triode, and Saturation

2 Exercise 1.5

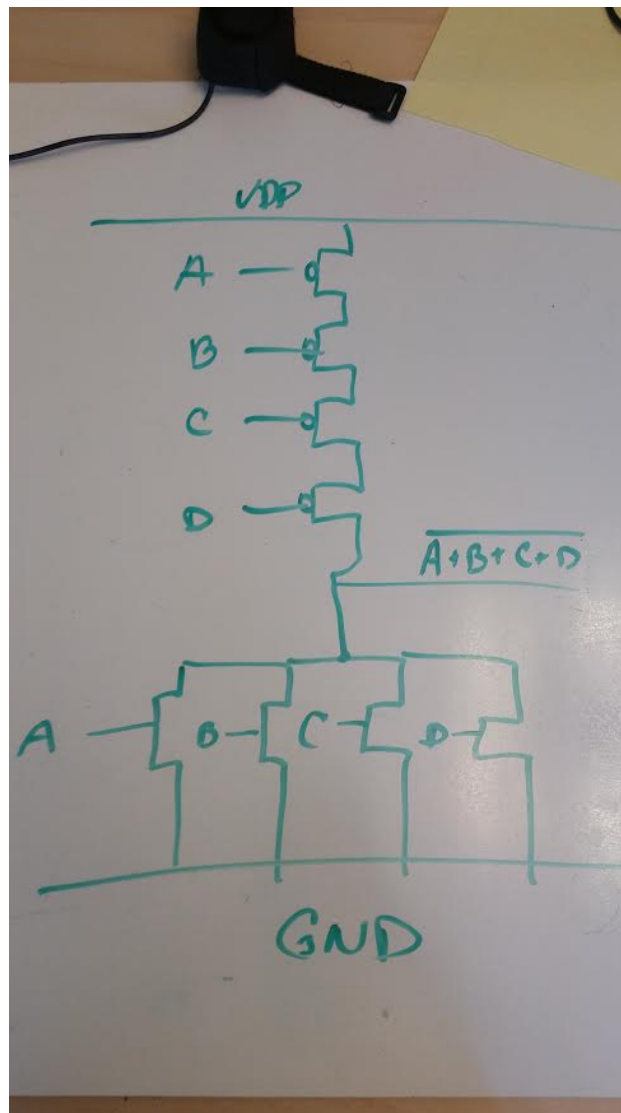


Figure 1: 4 Input NOR Gate

3 Exercise 1.3

a)

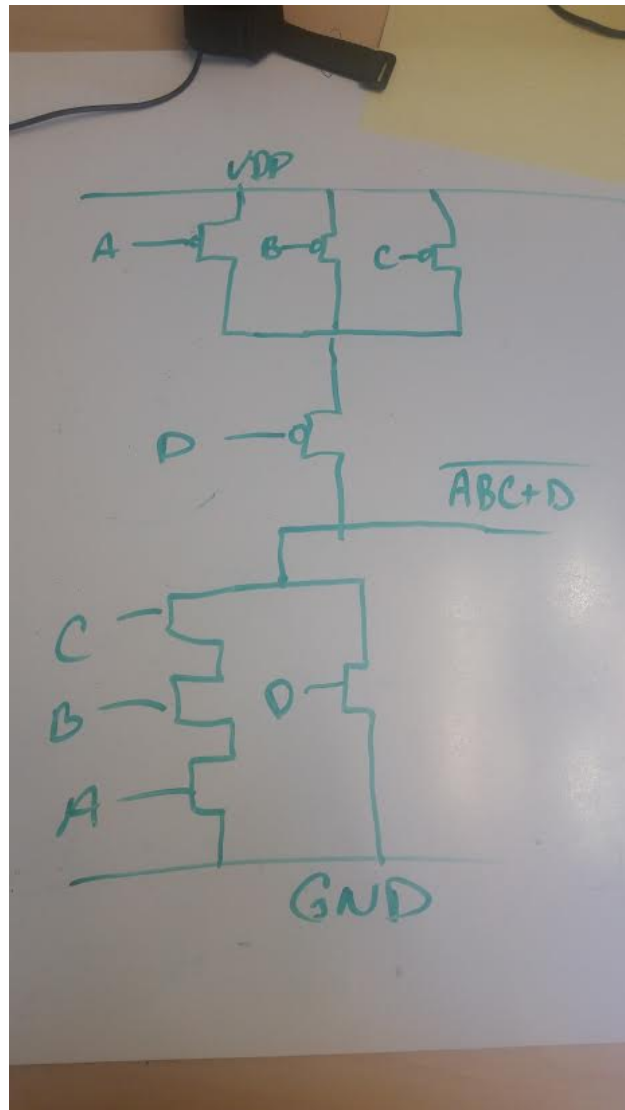


Figure 2: $\overline{ABC} + D$

b)

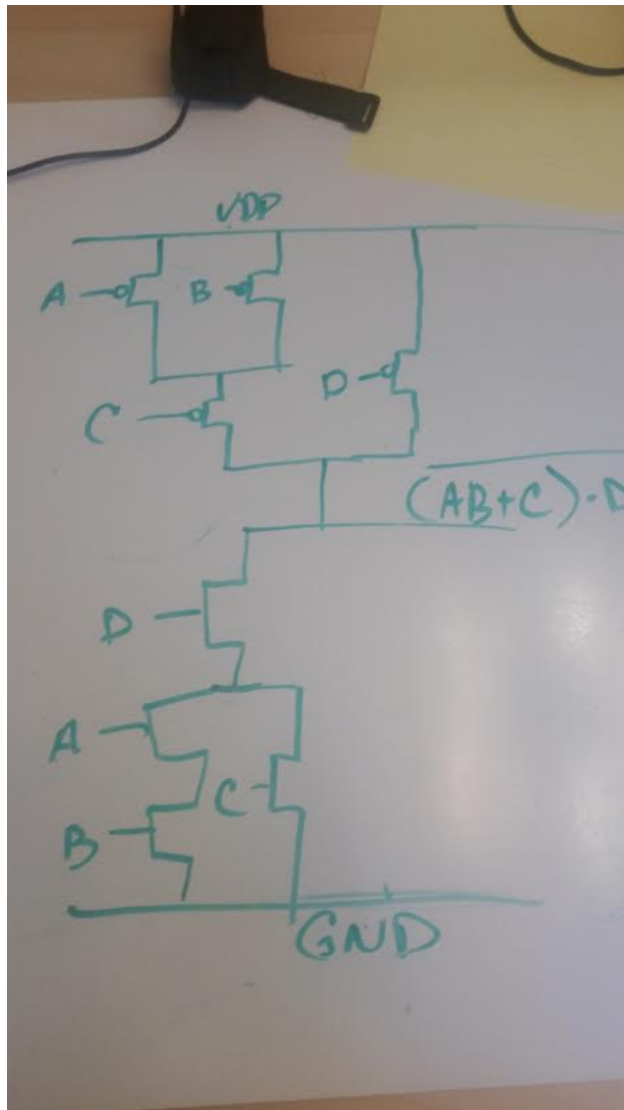


Figure 3: $\overline{(AB + C) \cdot D}$

c)

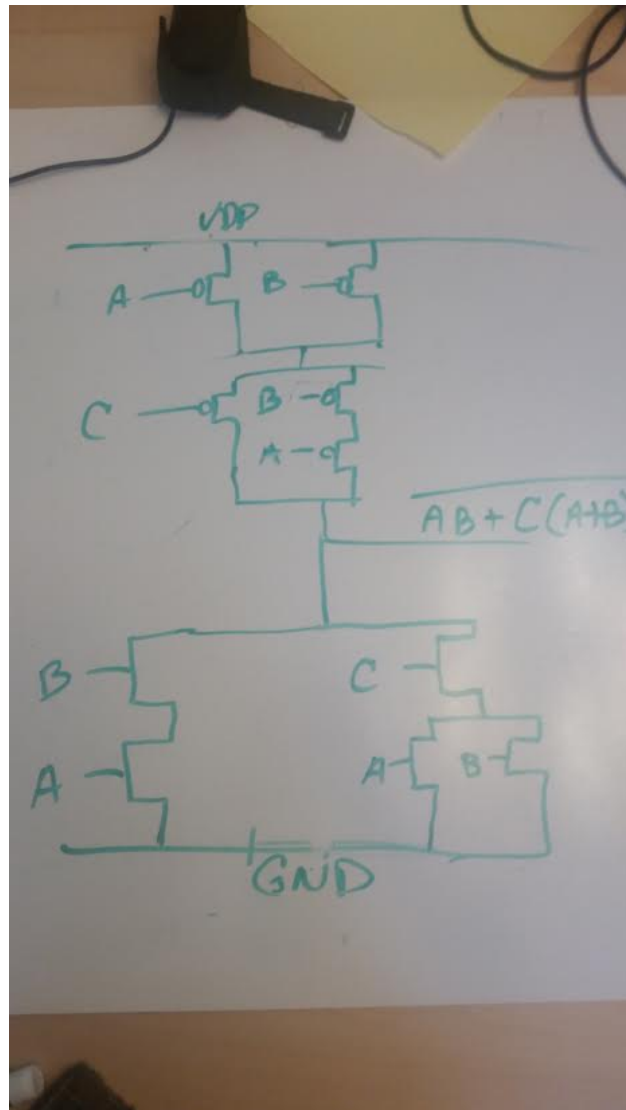


Figure 4: $\overline{AB + C(A+B)}$

4 Exercise 1.10

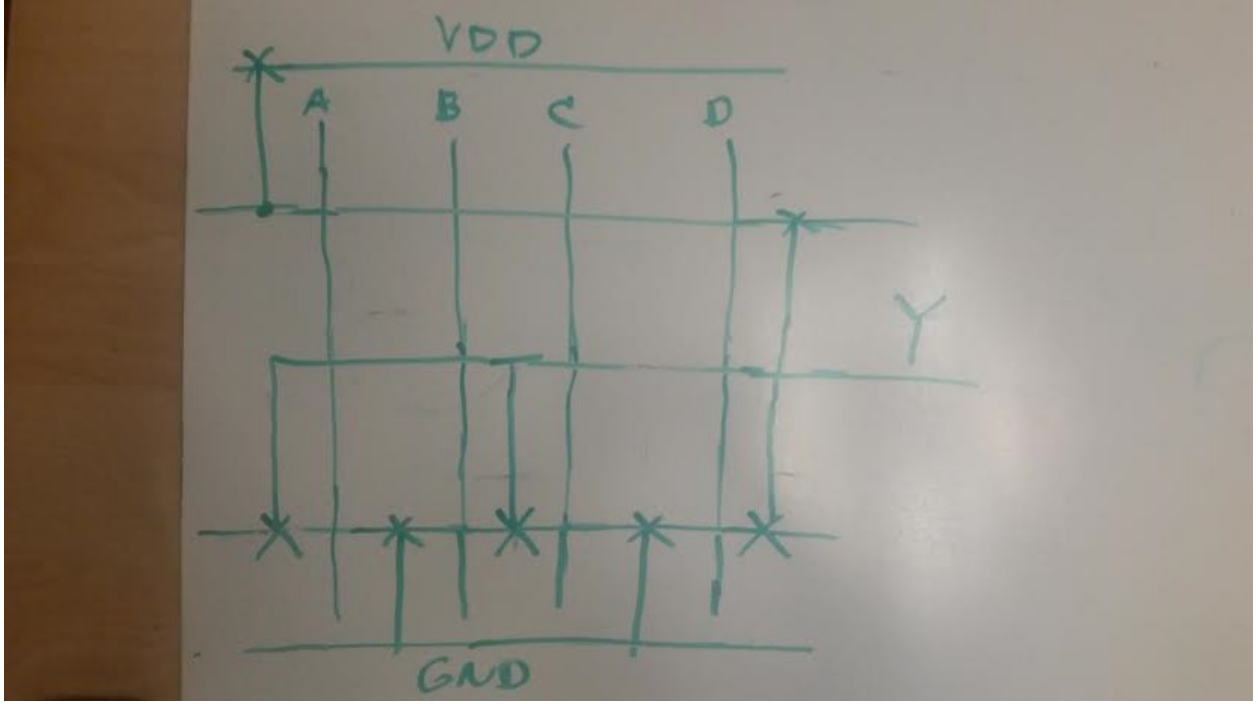


Figure 5: Stick Diagram for 4 Input NOR Gate

5 Exercise 2.2

Shockley Equation:

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{Cutoff} \\ \mu C_{ox} \frac{W}{L} (V_{GT} - 0.5V_{ds}) V_{ds} & V_{ds} < V_{dsat} & \text{Linear} \\ \mu C_{ox} \frac{W}{2L} V_{GT}^2 & V_{ds} > V_{dsat} & \text{Saturation} \end{cases}$$

Assuming the linear region, the current through the bottom transistor is:

$$\begin{aligned} I_{ds2} &= \mu C_{ox} \frac{W}{L} (V_{GT} - 0.5V_{ds}) V_{ds} \\ &= \mu C_{ox} \frac{W}{L} (V_{DD} - V_t - 0.5V_1) V_1 \end{aligned}$$

The current through the top transistor is:

$$\begin{aligned} I_{ds2} &= \mu C_{ox} \frac{W}{L} (V_{GT} - 0.5V_{ds}) V_{ds} \\ &= \mu C_{ox} \frac{W}{L} (V_{DD} - V_1 - V_t - 0.5(V_{ds} - V_1))(V_{ds} - V_1) \end{aligned}$$

Solving for V_1 , where V_1 is the voltage between the top and bottom transistors, we can obtain a quadratic expression:

$$\begin{aligned}
\mu C_{ox} \frac{W}{L} (V_{DD} - V_t - 0.5V_1)V_1 &= \mu C_{ox} \frac{W}{L} (V_{DD} - V_1 - V_t - 0.5(V_{ds} - V_1))(V_{ds} - V_1) \\
(V_{DD} - V_t - 0.5V_1)V_1 &= (V_{DD} - V_1 - V_t - 0.5(V_{ds} - V_1))(V_{ds} - V_1) \\
(V_{DD} - V_t)V_1 - 0.5V_1^2 &= (V_{DD} - V_t - 0.5V_{ds}) + 0.5V_1^2 - V_1(V_{DD} - V_t) \\
0 &= V_1^2 - 2V_1(V_{DD} - V_t) + V_{ds}(V_{DD} - 0.5V_{ds} - V_t) \\
V_1 &= \frac{2(V_{DD} - V_t) \pm \sqrt{4(V_{DD} - V_t)^2 - 4V_{ds}(V_{DD} - 0.5V_{ds} - V_t)}}{2}
\end{aligned}$$

Plugging V_1 into the original equation and doing a lot of tedious calculations we get:

$$I_{ds2} = \mu C_{ox} \frac{W}{2L} (V_{DD} - V_t - 0.5V_{ds})V_{ds}$$

The equation for I_{ds1} is:

$$I_{ds1} = \mu C_{ox} \frac{W}{2L} (V_{DD} - V_t - 0.5V_{ds})V_{ds}$$

Therefore the two currents are equivalent

6 Exercise 2.3

I_{ds2} will be less than I_{ds1} because in the case of having one transistor, $V_{sb} = 0$, however, when two transistors are in use, there is a voltage $V_{sb} \neq 0$ in the top transistor. The body effect will cause the threshold voltage to be greater than V_{to} , thus resulting in a lower value of I_{ds2} .

7 Exercise 2.7

Body Effect:

$$\begin{aligned}
V_t &= V_{to} + \gamma(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s}) \\
\gamma &= \frac{t_{ox}}{\epsilon_0 k_{ox}} \sqrt{2q\epsilon_{si}N_A} \\
\phi_s &= 2v_T \ln\left(\frac{N_A}{n_i}\right)
\end{aligned}$$

Solving for γ and ϕ_s :

$$\begin{aligned}
\phi_s &= 2(0.026) \ln \frac{2 \times 10^{17} \text{ cm}^{-3}}{1.45 \times 10^{10} \text{ cm}^{-3}} \approx 0.8548 \\
\gamma &= \frac{100 \times 10^{-8}}{3.9 \cdot 8.85 \times 10^{-14}} \sqrt{2(1.6 \times 10^{-19})(11.7)(8.85 \times 10^{-14})(2 \times 10^{17})} \approx 0.7458
\end{aligned}$$

Solving for the new threshold voltage we get:

$$V_t = 0.7 + 0.7458(\sqrt{0.8548 + 4} - \sqrt{0.8548}) \approx 1.653V$$

The voltage level changes by 0.95V

8 Exercise 2.9

A negative substrate bias should be used

9 Light Switch Design

Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	1	0
0	1	0	1
1	0	0	1
1	0	1	0
1	1	1	1
1	1	0	0

Karnaugh Map:

A \ BC	00	01	11	10
	0	1	0	1
0	0	1	0	1
1	1	0	1	0

a)

$$F = AB'C' + A'B'C + ABC + ABC'$$

 


Figure 6: NAND Gate Implementation

b)

$$F = (A + B + C)(A + B' + C')(A' + B + C')(A' + B' + C)$$

 


Figure 7: NOR Gate Implementation

10 CMOS Compound Gate

a)

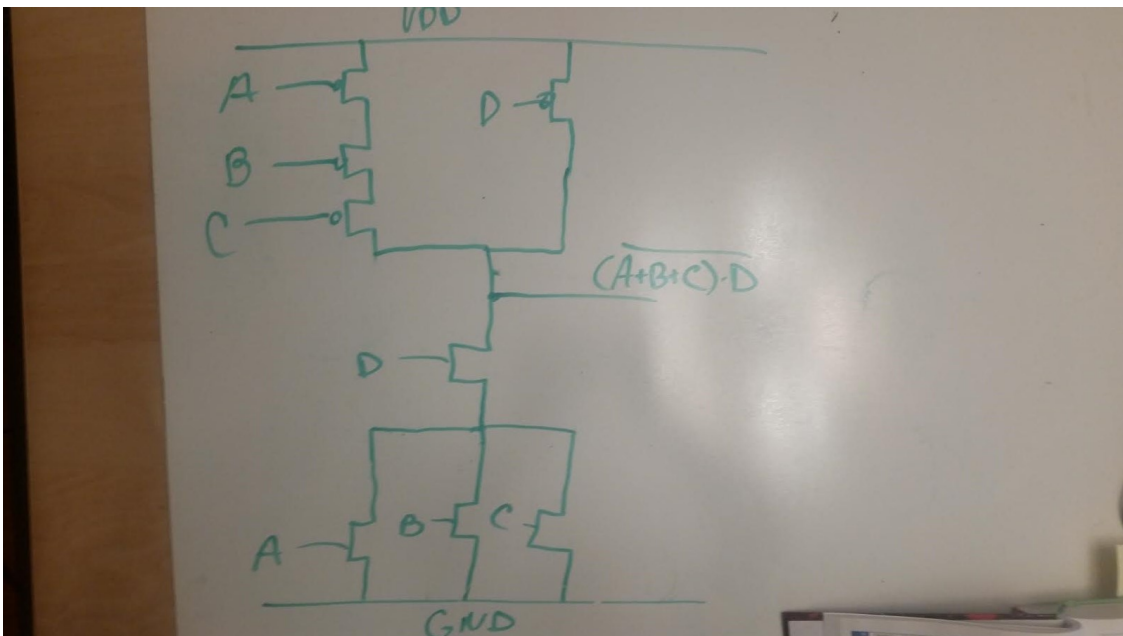


Figure 8: Transistor-Level Circuit

b)

 


Figure 9: Stick Diagram

c)

$$\text{Height} = 6 \text{ tracks} \times 8\lambda = 48\lambda$$

$$\text{Width} = 5 \text{ tracks} \times 8\lambda = 40\lambda$$